

## 第一章 课程实验一参考资料

对交大软件学院二年级-下的同学（2009 级），为深入理解计算机组成与设计的基本原理，培养从硬件和软件两方面全局考虑计算机针对问题求解所进行的系统设计思想，掌握针对一定规模系统的设计实践能力，配合课堂教学内容开设以下 3 个实验：

1. 单周期 CPU 设计实验；
2. 五段流水 CPU 设计实验；
3. 外部 I/O 及接口扩展实验。

### 1.1 实验一单周期 CPU 设计实验参考资料

#### 1.1.1 实验 DE2 板载资源：

（1）Altera-DE2 板载资源的详细介绍，参见 DE2\_UserManual.pdf。

（2）DE2 实验板不同于上学期的 JDEE-10K 教学实验箱，其上的 8 个 7 段 LED 数码管的连接电路采用每个段位直连到 FPGA 的 I/O 管脚的静态驱动方法，不是采用动态扫描的方式，如图 1-1 所示。详见 DE2\_UserManual.pdf 文档。

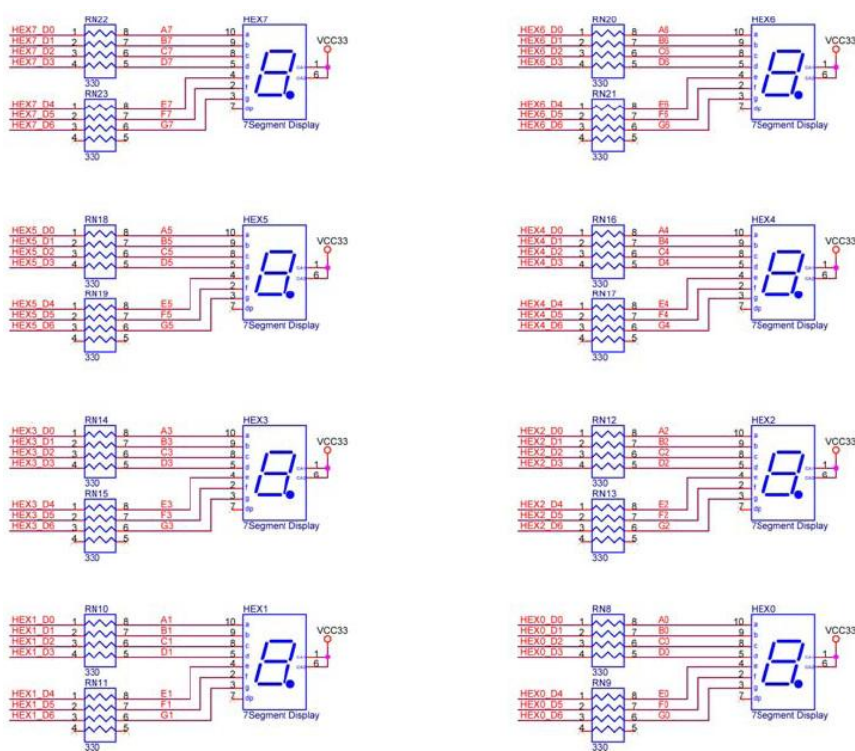


图 1-1. Altera-DE2 实验板上的 7 段 LED 数码管

（3）按键和拨动开关的连接电路详见 DE2\_UserManual.pdf 文档。

## 1.1.2. 部分原理介绍及辅助参考

MIPS指令格式										20 MIPS 指令																																													
<p><b>R 類型指令</b> (rs, rt, rd: 寄存器號, sa: 移位位數)</p> <table border="1"> <tr> <td>31</td><td>26</td><td>25</td><td>21</td><td>20</td><td>16</td><td>15</td><td>11</td><td>10</td><td>6</td><td>5</td><td>0</td> </tr> <tr> <td colspan="2">op</td> <td colspan="2">rs</td> <td colspan="2">rt</td> <td colspan="2">rd</td> <td colspan="2">sa</td> <td colspan="2">funct</td> </tr> <tr> <td colspan="2">6 bits</td> <td colspan="2">5 bits</td> <td colspan="2">5 bits</td> <td colspan="2">5 bits</td> <td colspan="2">5 bits</td> <td colspan="2">6 bits</td> </tr> </table>										31	26	25	21	20	16	15	11	10	6	5	0	op		rs		rt		rd		sa		funct		6 bits		5 bits		5 bits		5 bits		5 bits		6 bits		<pre> add rd, rs, rt ; rd &lt;-&gt; rs + rt sub rd, rs, rt ; rd &lt;-&gt; rs - rt and rd, rs, rt ; rd &lt;-&gt; rs &amp; rt or rd, rs, rt ; rd &lt;-&gt; rs   rt xor rd, rs, rt ; rd &lt;-&gt; rs ^ rt sll rd, rt, sa ; rd &lt;-&gt; rt &lt;&lt; sa srl rd, rt, sa ; rd &lt;-&gt; rt &gt;&gt; sa (logical) sra rd, st, sa ; rd &lt;-&gt; rt &gt;&gt; sa (arithmetic) jr rs ; PC &lt;-&gt; rs  addi rt, rs, imm ; rt &lt;-&gt; rs + (sign)imm andi rt, rs, imm ; rt &lt;-&gt; rs &amp; (zero)imm ori rt, rs, imm ; rt &lt;-&gt; rs   (zero)imm xori rt, rs, imm ; rt &lt;-&gt; rs ^ (zero)imm lw rt, imm(rs) ; rt &lt;-&gt; memory[rs + (sign)imm] sw rt, imm(rs) ; memory[rs + (sign)imm] &lt;-&gt; rt beq rs, rt, imm ; if (rs == rt) PC &lt;-&gt; PC + 4 + (sign)imm &lt;&lt; 2 bne rs, rt, imm ; if (rs != rt) PC &lt;-&gt; PC + 4 + (sign)imm &lt;&lt; 2 lui rt, imm ; rt &lt;-&gt; imm &lt;&lt; 16  j addr ; PC &lt;-&gt; (PC+4)[31..28], addr &lt;&lt; 2 jal addr ; \$31 &lt;-&gt; PC+4; PC &lt;-&gt; (PC+4)[31..28], addr &lt;&lt; 2 </pre>									
31	26	25	21	20	16	15	11	10	6	5	0																																												
op		rs		rt		rd		sa		funct																																													
6 bits		5 bits		5 bits		5 bits		5 bits		6 bits																																													
<p><b>I 類型指令</b> (rs, rt: 寄存器號, imm: 立即數)</p> <table border="1"> <tr> <td>31</td><td>26</td><td>25</td><td>21</td><td>20</td><td>16</td><td>15</td><td>0</td> </tr> <tr> <td colspan="2">op</td> <td colspan="2">rs</td> <td colspan="2">rt</td> <td colspan="6">imm</td> </tr> <tr> <td colspan="2">6 bits</td> <td colspan="2">5 bits</td> <td colspan="2">5 bits</td> <td colspan="6">16 bits</td> </tr> </table>										31	26	25	21	20	16	15	0	op		rs		rt		imm						6 bits		5 bits		5 bits		16 bits																			
31	26	25	21	20	16	15	0																																																
op		rs		rt		imm																																																	
6 bits		5 bits		5 bits		16 bits																																																	
<p><b>J 類型指令</b> (addr: 跳轉目標地址)</p> <table border="1"> <tr> <td>31</td><td>26</td><td>25</td><td colspan="8">0</td> </tr> <tr> <td colspan="2">op</td> <td colspan="10">addr</td> </tr> <tr> <td colspan="2">6 bits</td> <td colspan="10">26 bits</td> </tr> </table>										31	26	25	0								op		addr										6 bits		26 bits																				
31	26	25	0																																																				
op		addr																																																					
6 bits		26 bits																																																					

© YAMIN LI, CIS, HOSEI UNIVERSITY Single-Cycle CPU Design – p.8/79 © YAMIN LI, CIS, HOSEI UNIVERSITY Single-Cycle CPU Design – p.9/79


20 MIPS 指令										單周期 CPU + 指令存儲器 + 數據存儲器									
<p>op rs rt rd sa funct ; R format instructions</p> <pre> 000000 rs rt rd 00000 100000 ; add rd, rs, rt 000000 rs rt rd 00000 100010 ; sub rd, rs, rt 000000 rs rt rd 00000 100100 ; and rd, rs, rt 000000 rs rt rd 00000 100101 ; or rd, rs, rt 000000 rs rt rd 00000 100110 ; xor rd, rs, rt 000000 00000 rt rd sa 000000 ; sll rd, rt, sa 000000 00000 rt rd sa 000010 ; srl rd, rt, sa 000000 00000 rt rd sa 000011 ; sra rd, st, sa 000000 rs 00000 00000 00000 001000 ; jr rs  001000 rs rt imm ; addi rt, rs, imm 001100 rs rt imm ; andi rt, rs, imm 001101 rs rt imm ; ori rt, rs, imm 001110 rs rt imm ; xori rt, rs, imm 100011 rs rt imm ; lw rt, imm(rs) 101011 rs rt imm ; sw rt, imm(rs) 000100 rs rt imm ; beq rs, rt, imm 000101 rs rt imm ; bne rs, rt, imm 001111 00000 rt imm ; lui rt, imm  op addr ; J format instructions 000010 addr ; j addr 000011 addr ; jal addr </pre>										<p>Legend: 0: PC+4 1: BranchAddr 2: RegAddr 3: JumpAddr</p>									

© YAMIN LI, CIS, HOSEI UNIVERSITY Single-Cycle CPU Design – p.10/79 © YAMIN LI, CIS, HOSEI UNIVERSITY Single-Cycle CPU Design – p.17/79

add, sub, and, or, xor 指令										sll, srl, sra 指令									
<p>add, sub, and, or, xor add rd, rs, rt</p>										<p>sll, srl, sra sll rd, rt, sa</p>									

© YAMIN LI, CIS, HOSEI UNIVERSITY Single-Cycle CPU Design – p.41/79 © YAMIN LI, CIS, HOSEI UNIVERSITY Single-Cycle CPU Design – p.42/79


### lui 指令

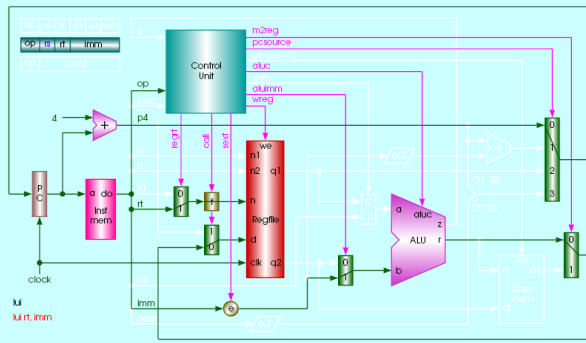

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.43/79


### addi, andi, ori, xori 指令

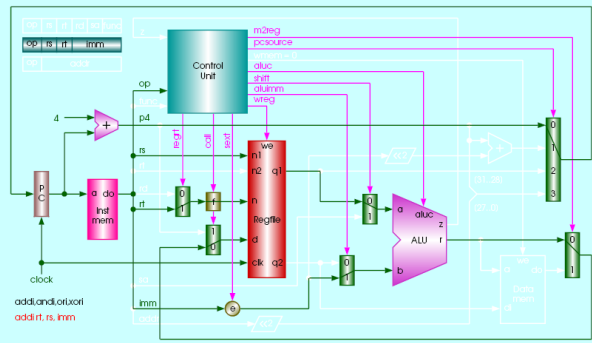

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.44/79


### lw 指令

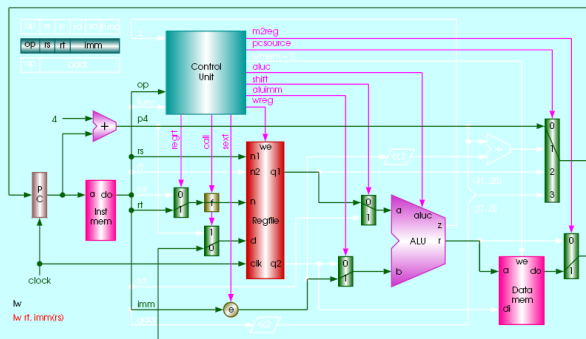

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.45/79


### sw 指令

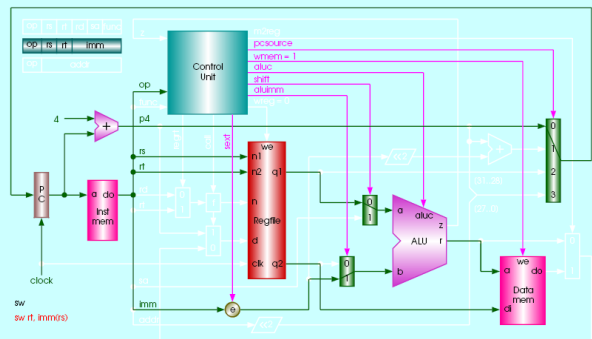

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.46/79


### beq, bne 指令

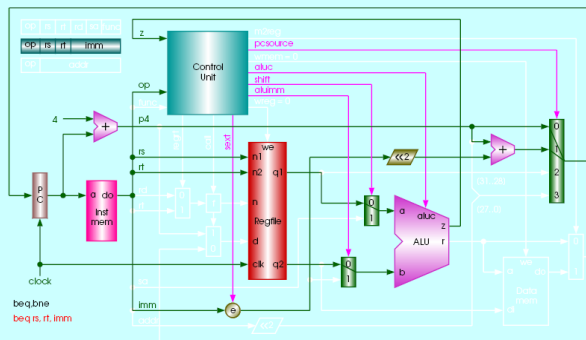

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.47/79


### jr 指令

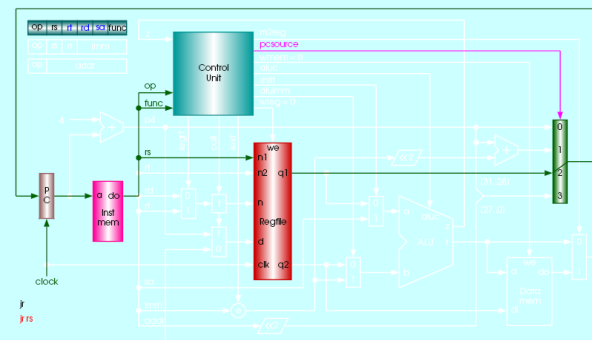

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.48/79


## j 指令

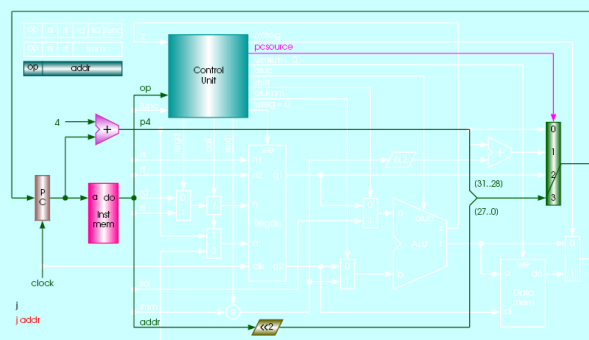

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.49/79

## jal 指令

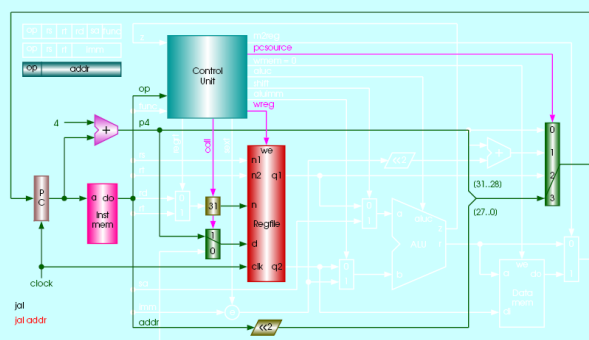

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.50/79

## 控制部件

MIPS CPU 指令格式


R 類型指令



I 類型指令



J 類型指令

 

## 控制信號的種類

1. 寫使能 (Write Enable)

- wreg
- wmem

2. ALU操作控制

- aluc(3..0)

3. 多路器的選擇信號

- m2reg
- pcsource(1..0)
- shift
- aluimm
- regrt
- call
- sext

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.52/79

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.53/79

## 控制信號的意義

- wreg
  - 1: 寫寄存器堆
  - 0: 不寫
- wmem
  - 1: 寫存儲器
  - 0: 不寫
- m2reg
  - 1: 選擇從存儲器中讀出的數據
  - 0: 選擇ALU的運算結果
- shift
  - 1: 選擇移位位數(sa)
  - 0: 選擇寄存器堆的數據

## 控制信號的意義

- aluimm
  - 1: 選擇擴展後的立即數
  - 0: 選擇寄存器堆的數據
- regrt
  - 1: 選擇rt
  - 0: 選擇rd
- call
  - 1: 選擇PC+4
  - 0: 選擇ALU或者存儲器數據
- sext
  - 1: 符號擴展
  - 0: 零擴展

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.54/79

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.55/79

## 控制信號的意義

- pccsource(1..0)
  - 0 0: 選擇PC+4
  - 0 1: 選擇轉移地址
  - 1 0: 選擇寄存器地址
  - 1 1: 選擇跳轉地址
- aluc(3..0)
  - x 0 0 0: ADD (指令: add, addi, lw, sw)
  - x 1 0 0: SUB (指令: sub, beq, bne)
  - x 0 0 1: AND (指令: and, andi)
  - x 1 0 1: OR (指令: or, ori)
  - x 0 1 0: XOR (指令: xor, xori)
  - x 1 1 0: LUI (指令: lui)
  - 0 0 1 1: SLL (指令: sll)
  - 0 1 1 1: SRL (指令: srl)
  - 1 1 1 1: SRA (指令: sra)

## 控制部件設計

首先確認是什麼指令, 即對指令進行譯碼

R 類型			I 類型	
指令	op(5..0)	func(5..0)	指令	op(5..0)
add	000000	100000	addi	001000
sub	000000	100010	andi	001100
and	000000	100100	ori	001101
or	000000	100101	xori	001110
xor	000000	100110	lw	100011
sll	000000	000000	sw	101011
srl	000000	000010	beq	000100
sra	000000	000011	bne	000101
jr	000000	001000	lui	001111

J 類型			
指令	op(5..0)	指令	op(5..0)
j	000010	jal	000011

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.56/79

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.58/79

## 指令譯碼

生成表示指令的中間變量, 變量名與指令名相同<sup>a</sup>

```

Rtype = op(5) · op(4) · op(3) · op(2) · op(1) · op(0)
add = Rtype · func(5) · func(4) · func(3) · func(2) · func(1) · func(0)
sub = Rtype · func(5) · func(4) · func(3) · func(2) · func(1) · func(0)
... = ...

addi = op(5) · op(4) · op(3) · op(2) · op(1) · op(0)
... = ...

j = op(5) · op(4) · op(3) · op(2) · op(1) · op(0)
jal = op(5) · op(4) · op(3) · op(2) · op(1) · op(0)

```

<sup>a</sup>在 Verilog HDL 中不能這樣幹, 因為有些指令名與 Verilog HDL 關鍵字相同

## 控制部件設計

然後, 寫出控制信號的邏輯表達式

輸入	輸出									
指令	z	pccsource(1..0)	aluc(3..0)	shift	alumm	sext	wmem	wreg	m2reg	regt
add	x	0 0	0 0 0 0	0	0	x	0	1	0	0
...	x									
sll	x	0 0	0 0 1 1	1	0	x	0	1	0	0
...	x									
beq	0	0 0						0		
...	1	0 1								
...	x									
j	x	1 1	x x x x	x	x	x	0	0	x	x
jal	x	1 1	x x x x	x	x	x	0	1	x	x

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.59/79

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.61/79

## 控制部件設計

控制信號的邏輯表達式

```

pccsource(1) =
pccsource(0) =
  aluc(3) =
  aluc(2) =
  aluc(1) =
  aluc(0) =
  ... =
  wmem = st;
  wreg = add + sub + and + or + xor + sll + srl + sra +
    addi + andi + ori + xori + lw + lui + jal;
  ... =
  call = jal;

```

## 測試程序

```

DEPTH = 64;          % Memory depth and width are required %
WIDTH = 32;          % Enter a decimal number %
ADDRESS_RADIX = HEX; % Address and value radices are optional %
DATA_RADIX = HEX;    % Enter BIN, DEC, HEX, or OCT; unless %
                     % otherwise specified, radices = HEX %

CONTENT
BEGIN
  0 : 3c010000; % (00)   main:  lui $1, 0          # address of data[0] %
  1 : 34240050; % (04)   ori  $4, $1, 80         # address of data[0] %
  2 : 20050004; % (08)   addi $5, $0, 4          # counter %
  3 : 0c000018; % (0c)   call:  jal sum          # call function %
  4 : ac820000; % (10)   sw  $2, 0($4)          # store result %
  5 : 8c890000; % (14)   lw  $9, 0($4)          # check sw %
  6 : 01244022; % (18)   sub  $8, $9, $4        # sub: $8 <- $9 - $4 %
  7 : 20050003; % (1c)   addi $5, $0, 3          # counter %
  8 : 20a5ffff; % (20)   loop2: addi $5, $5, -1   # counter - 1 %
  9 : 34a8ffff; % (24)   ori  $8, $5, 0xffff     # zero-extend: 0000ffff %
  A : 39085555; % (28)   xori $8, $8, 0x5555    # zero-extend: 0000aaaa %
  B : 2009ffff; % (2c)   addi $9, $0, -1        # sign-extend: ffffffff %
  C : 312affff; % (30)   andi $10, $9, 0xffff   # zero-extend: 0000ffff %

```

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.62/79

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.67/79

## 測試程序

```

D : 01493025; % (34)      or $6, $10, $9      # or: ffffffff %
E : 01494026; % (38)      xor $8, $10, $9      # xor: ffff0000 %
F : 01463824; % (3c)      and $7, $10, $6      # and: 0000ffff %
10 : 10a00001; % (40)      beq $5, $0, shift    # if $5 = 0, goto shift %
11 : 08000008; % (44)      j loop2            # jump loop2 %
12 : 2005ffff; % (48)      shift: addi $5, $0, -1 # $5 = ffffffff %
13 : 000543c0; % (4c)      sll $8, $5, 15      # <15 = ffff8000 %
14 : 00084400; % (50)      sll $8, $8, 16      # <16 = 80000000 %
15 : 00084403; % (54)      sra $8, $8, 16      # >16 = ffff8000 (arith) %
16 : 000843c2; % (58)      srl $8, $8, 15      # >15 = 0001ffff (logic) %
17 : 08000017; % (5c)      finish: j finish      # dead loop %
18 : 00004020; % (60)      sum: add $8, $0, $0      # sum %
19 : 8c890000; % (64)      loop: lw $9, 0($4)      # load data %
1A : 20840004; % (68)      addi $4, $4, 4        # address + 4 %
1B : 01094020; % (6c)      add $8, $8, $9        # sum %
1C : 20a5ffff; % (70)      addi $5, $5, -1        # counter - 1 %
1D : 14a0ffff; % (74)      bne $5, $0, loop      # finish? %
1E : 00081000; % (78)      sll $2, $8, 0        # move result to $v0 %
1F : 03a00008; % (7c)      jr $ra              # return %
END ;


```

## 測試數據和模擬波形

```

DEPTH = 32; % Memory depth and width are required %
WIDTH = 32; % Enter a decimal number %
ADDRESS_RADIX = HEX; % Address and value radices are optional %
DATA_RADIX = HEX; % Enter BIN, DEC, HEX, or OCT; unless %
CONTENT % otherwise specified, radices = HEX %
BEGIN
  14 : 000000A3; % (50) data[0] %
  15 : 00000027; % (54) data[1] %
  16 : 00000079; % (58) data[2] %
  17 : 00000115; % (5C) data[3] %
END ;

```

 



© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.68/79

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.69/79



## 模擬波形

  

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.70/79

## 模擬波形

  

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.71/79

顶层代码结构，实验中具体指令 ROM 存储器和数据 RAM 存储器的实现方法有所不同。注意采用 Altera 宏模块进行实现时的差异。

## Example: sc\_comp.v

```

module sc_comp (clock, resetn, inst, pc, aluout, memout, mem_clk);
  input clock, resetn, mem_clk;
  output [31:0] inst, pc, aluout, memout;
  wire [31:0] data;
  wire wmem;
  sc_cpu cpu (clock, resetn, inst, memout, pc, wmem, aluout, data);
  scinstmem imem (pc, inst);
  scdatamem dmem (clock, memout, data, aluout, wmem, mem_clk, mem_clk);
endmodule

```

© YAMIN LI, CIS, HOSEI UNIVERSITY

Single-Cycle CPU Design – p.73/79